



- ① $\sum i @ V_1 \quad i_1 = i_2 + i_4$
- ② $\sum i @ V_2 \quad i_2 = i_3 + i_5$
- ③ $\sum i @ V_3 \quad i_4 = i_6 + i_{11}$
- ④ $\sum i @ V_4 \quad i_5 + i_{11} = i_7 + i_{12}$
- ⑤ $\sum i @ V_5 \quad i_3 + i_{12} + i_{10} = 0$
- ⑥ $\sum i @ V_6 \quad i_6 = i_8 + i_9$
- ⑦ $\sum i @ V_7 \quad i_7 + i_9 = i_{10}$

$$i_1 = \frac{10 - V_1}{R_1} \quad i_2 = \frac{V_1 - V_2}{R_2} \quad i_3 = \frac{V_2 - V_5}{R_3}$$

$$i_4 = \frac{V_1 - V_3}{R_4} \quad i_5 = \frac{V_2 - V_4}{R_5} \quad i_6 = \frac{V_3 - V_6}{R_6}$$

$$i_7 = \frac{V_4 - V_7}{R_7} \quad i_8 = \frac{V_6}{R_8} \quad i_9 = \frac{V_6 - V_7}{R_9}$$

$$i_{10} = \frac{V_7 - V_5}{R_{10}} \quad i_{11} = \frac{V_3 - V_4}{R_{11}} \quad i_{12} = \frac{V_4 - V_5}{R_{12}}$$

$$\textcircled{1} \quad \frac{V_0 - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_3}{R_4}$$

$$\textcircled{2} \quad \frac{V_1 - V_2}{R_2} = \frac{V_2 - V_5}{R_3} + \frac{V_2 - V_4}{R_5}$$

$$\textcircled{3} \quad \frac{V_1 - V_3}{R_4} = \frac{V_3 - V_6}{R_6} + \frac{V_3 - V_4}{R_{11}}$$

$$\textcircled{4} \quad \frac{V_2 - V_4}{R_5} + \frac{V_3 - V_4}{R_{11}} = \frac{V_4 - V_7}{R_7} + \frac{V_4 - V_5}{R_{12}}$$

$$\textcircled{5} \quad \frac{V_2 - V_5}{R_3} + \frac{V_4 - V_5}{R_{12}} + \frac{V_7 - V_5}{R_{10}} = 0$$

$$\textcircled{6} \quad \frac{V_3 - V_6}{R_6} = \frac{V_6}{R_8} + \frac{V_6 - V_7}{R_9}$$

$$\textcircled{7} \quad \frac{V_4 - V_7}{R_7} + \frac{V_6 - V_7}{R_9} = \frac{V_7 - V_5}{R_{10}}$$

If all of the resistors are the same 1kΩ, then we can simplify

$$\textcircled{1} \quad 10 - v_1 = v_1 - v_2 + v_1 - v_3$$

$$\checkmark 3v_1 - v_2 - v_3 + 0v_4 + 0v_5 + 0v_6 + 0v_7 = 10$$

$$\textcircled{2} \quad v_1 - v_2 = v_2 - v_5 + v_2 - v_4$$

$$\checkmark v_1 - 3v_2 + 0v_3 + v_4 + v_5 + 0v_6 + 0v_7 = 0$$

$$\textcircled{3} \quad v_1 - v_3 = v_3 - v_6 + v_3 - v_4$$

$$\checkmark v_1 + 0v_2 - 3v_3 + v_4 + 0v_5 + v_6 + 0v_7 = 0$$

$$\textcircled{4} \quad v_2 - v_4 + v_3 - v_4 = v_4 - v_7 + v_4 - v_5$$

$$\checkmark 0v_1 + v_2 + v_3 - 4v_4 + v_5 + 0v_6 + v_7 = 0$$

$$\textcircled{5} \quad v_2 - v_5 + v_4 - v_5 + v_7 - v_5 = 0$$

$$\checkmark 0v_1 + v_2 + 0v_3 + v_4 - 3v_5 + 0v_6 + v_7 = 0$$

$$\textcircled{6} \quad v_3 - v_6 = v_6 + v_6 - v_7$$

$$\checkmark 0v_1 + 0v_2 + v_3 + 0v_4 + 0v_5 - 3v_6 + v_7 = 0$$

$$\textcircled{7} \quad v_4 - v_7 + v_6 - v_7 = v_7 - v_5$$

$$\checkmark 0v_1 + 0v_2 + 0v_3 + v_4 + v_5 + v_6 - 3v_7 = 0$$

$$\left[\begin{array}{ccccccc} 3 & -1 & -1 & 0 & 0 & 0 & 0 \\ 1 & -3 & 0 & 1 & 1 & 0 & 0 \\ 1 & 0 & -3 & 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & -4 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 & -3 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & -3 & 1 \\ 0 & 0 & 0 & 1 & 1 & 1 & -3 \end{array} \right] \left[\begin{array}{c} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \end{array} \right] = \left[\begin{array}{c} 10 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right]$$

» A USING MATLAB TO SOLVE, WE GET THE FOLLOWING:

A =

3	-1	-1	0	0	0	0
1	-3	0	1	1	0	0
1	0	-3	1	0	1	0
0	1	1	-4	1	0	1
0	1	0	1	-3	0	1
0	0	1	0	0	-3	1
0	0	0	1	1	1	-3

» b

b =

10
0
0
0
0
0
0

» x=A\b

x =

6.8750 — v₁
5.6250 — v₂
5.0000 — v₃
5.0000 — v₄
5.0000 — v₅
3.1250 — v₆
4.3750 — v₇

»

CARL, I SHOULD OF HAD A V8 :-)

OR, WE CAN USE PSPICE TO SIMULATE THE CIRCUIT

